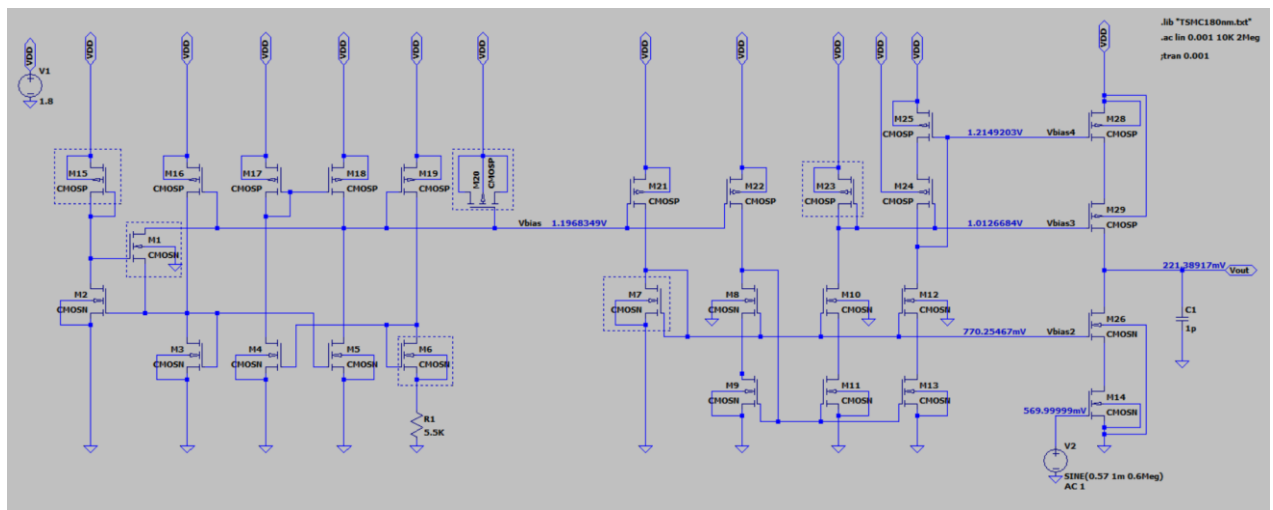


Indian Institute of Technology Ropar

EE301: Analog Circuits

180NM:

The LTspice schematic for the 180nm circuit:



TRANSISTOR PARAMETERS	W/L	N-CHANNEL	P-CHANNEL	UNITS
MINIMUM	0.27/0.18			
Vth		0.50	-0.51	volts
SHORT	20.0/0.18			
Idss		547	-250	uA/um
Vth		0.51	-0.51	volts
Vpt		4.8	-5.6	volts
WIDE	20.0/0.18			
Ids0		14.4	-4.7	pA/um
LARGE	50/50			
Vth		0.43	-0.42	volts
Vjbkd		3.1	-4.3	volts
Ijlk		<50.0	<50.0	pA
K' (Uo*Cox/2)		175.4	-35.6	uA/V^2
Low-field Mobility		416.52	84.54	cm^2/V*s

The image above is taken from the provided 180nm_file_information.txt file.

Here we can see that the values are given as:

For NMOS:

$$U_n C_{ox} = 175.4 * 2 = 350.8 \text{ uA/V}^2$$

$$\text{Threshold Voltage } V_{th} = 0.5 \text{ V}$$

For PMOS:

$$U_p C_{ox} = -35.6 * 2 = -71.2 \text{ uA/V}^2$$

$$\text{Threshold Voltage } V_{th} \approx -0.5 \text{ V}$$

Lets, assume the frequency to be $F = 0.6\text{MHz}$ or 600KHz

$$\text{And we know that: } F = \frac{1}{2\pi * C * R_{out}}$$

Capacitance is given as $C = 1\text{pF}$

Putting the values of F and C we get $R_{out} = 265393 \text{ K}\Omega$

$$\text{And Voltage gain } A_v = g_m * R_{out}$$

As per the target specifications, $A_v = 20$ or 26dB

$$\text{So, we get } g_m = \frac{A_v}{R_{out}} = 75.3 \text{ }\mu\text{A/V}$$

For NMOS:

$$\text{In saturation, the current equation is: } I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} V_{ov}^2$$

$$\text{Where } V_{ov} = V_{gs} - V_{th}$$

For NMOS:

$$\text{In saturation, the current equation is: } I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} V_{ov}^2$$

Where

$$V_{ov} = V_{gs} - V_{th}$$

$$V_{gs} \geq V_{th} \quad \& \quad V_{ds} \geq V_{gs} - V_{th}$$

We can get the swing as:


$$V_g \geq V_{th} - V_s \quad \& \quad V_g \leq V_{th} + V_{th}$$

Assuming $V_{ds \text{ sat}} = 0.2\text{V}$

For Amplifier, I got the swing as (using $V_{th} = 0.5$ & $V_{ds \text{ min}}$ or $V_{ds \text{ sat}} = 0.2$) :

 1. M14: $0.5 - 0.7$
2. M26: $0.7 - 0.9$
3. M29: $0.9 - 1.1$
4. M28: $1.1 - 1.3$

Now ran a DC sweep from 0V to 1.8V to get the V_{bias1} :



From the graph it can be clearly seen that the $V_{bias1} = 0.57V$

Now, taking biasing voltages in the voltage swing range to ensure operation of all mosfet in saturation region.

We checked for different values of corresponding bias voltages V_{bias2} , V_{bias3} and V_{bias4} and W/L ratios according to bias voltages to get the 26dB gain.


And got the values as:

$$V_{bias1} = 0.57V, \quad W/L = 3.7$$

$$V_{bias2} = 0.77V, \quad W/L = 3.7$$


$$V_{bias3} = 1.01V, \quad W/L = 10.4$$

$$V_{bias4} = 1.21V, \quad W/L = 10.4$$

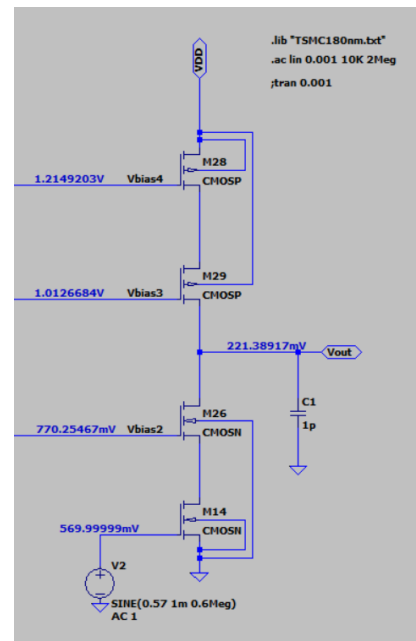

Observations:


Input Voltage:

 

We have given input bias voltage or DC offset = 0.57V and small signal AC voltage amplitude = 1mV.

So the peak-peak input voltage = 2mV

Output Voltage:

 

Got the output as $V_{max} = 243\text{mV}$ & $V_{min} = 203\text{mV}$.

So peak-peak = 40mV .

So voltage gain = $(\text{peak-peak output})/(\text{peak-peak input}) = 40/2 = 20 \text{ V/V}$


Gain vs Frequency:



Can be seen from the frequency curve as well that is shown above that the gain comes out to be 26dB that is 20V/V .

22NM:

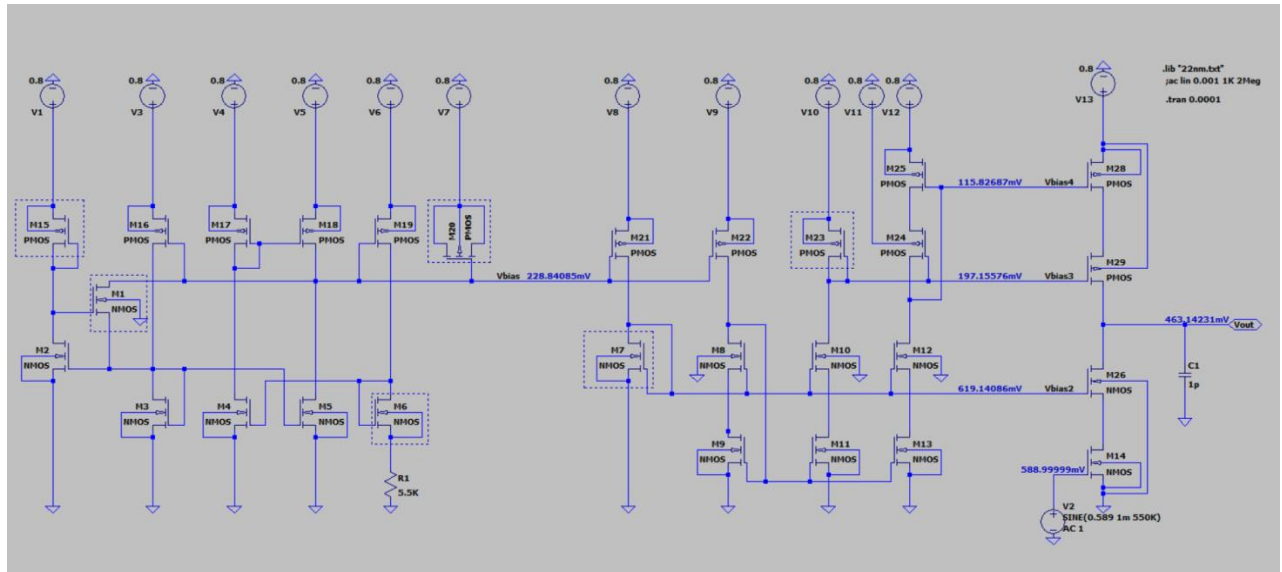The LTspice schematic for the 22nm circuit:



Since the information file for 22nm was not provided, so I searched on google to get the values for 22nm and got a range of values so took the mid values as shown below.

For NMOS:

$$U_n C_{ox} = 100 - 200(\text{range}) \approx 150 \mu\text{A}/\text{V}^2$$

$$\text{Threshold Voltage } V_{th} = 0.2 - 0.4 \approx 0.3\text{V}$$

For PMOS:

$$U_p C_{ox} = 50 - 100(\text{range}) = -70 \mu\text{A}/\text{V}^2$$

$$\text{Threshold Voltage } V_{th} \approx -0.3\text{V}$$

Lets, assume the frequency to be $F = 0.550\text{MHz}$ or 550KHz

$$\text{And we know that: } F = \frac{1}{2\pi * C * R_{out}}$$

Capacitance is given as $C = 1\text{pF}$

Putting the values of F and C we get $R_{out} = 289519\text{K}\Omega$

And Voltage gain $A_v = g_m * R_{out}$

As per the target specifications, $A_v = 20$ or 26dB

$$\text{So, we get } g_m = \frac{A_v}{R_{out}} = 69 \mu\text{A}/\text{V}$$

For NMOS:

$$\text{In saturation, the current equation is: } I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} V_{ov}^2$$

$$\text{Where } V_{ov} = V_{gs} - V_{th}$$

For NMOS:

In saturation, the current equation is: $I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} V_{ov}^2$

Where


$$V_{ov} = V_{gs} - V_{th}$$

$$V_{gs} \geq V_{th} \quad \& \quad V_{ds} \geq V_{gs} - V_{th}$$

We can get the swing as:

$$V_g \geq V_{th} - V_s \quad \& \quad V_g \leq V_{th} + V_{th}$$

 Now ran a DC sweep from 0V to 1.8V to get the V_{bias1} :



From the graph it can be clearly seen that the $V_{bias1} = 0.589V$

Now, taking biasing voltages in the voltage swing range to ensure operation of all mosfet in saturation region.

We checked for different values of corresponding bias voltages V_{bias2} , V_{bias3} and V_{bias4} and W/L ratios according to bias voltages to get the 26dB gain.


And got the values as:

$$V_{bias1} = 0.589V, \quad W/L = 8.1$$

$$V_{bias2} = 0.619V, \quad W/L = 8.1$$


$$V_{bias3} = 0.197V, \quad W/L = 17$$

$$V_{bias4} = 0.115V, \quad W/L = 17$$

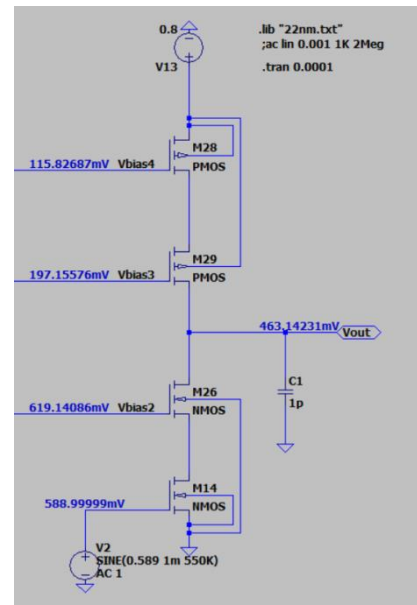

Observations:


Input Voltage:

 

We have given input bias voltage or DC offset = 0.589V and small signal AC voltage amplitude = 1mV.

So the peak-peak input voltage = 2mV

Output Voltage:

 


Got the output as $V_{max} = 482\text{mV}$ & $V_{min} = 442\text{mV}$.

So peak-peak = 40mV.

So voltage gain = $(\text{peak-peak output})/(\text{peak-peak input}) = 40/2 = 20 \text{ V/V}$


Gain vs Frequency:

 




Can be seen from the frequency curve as well that is shown above that the gain comes out to be 26dB that is 20V/V.

MAGIC LAYOUT:


Cascode Amplifier:

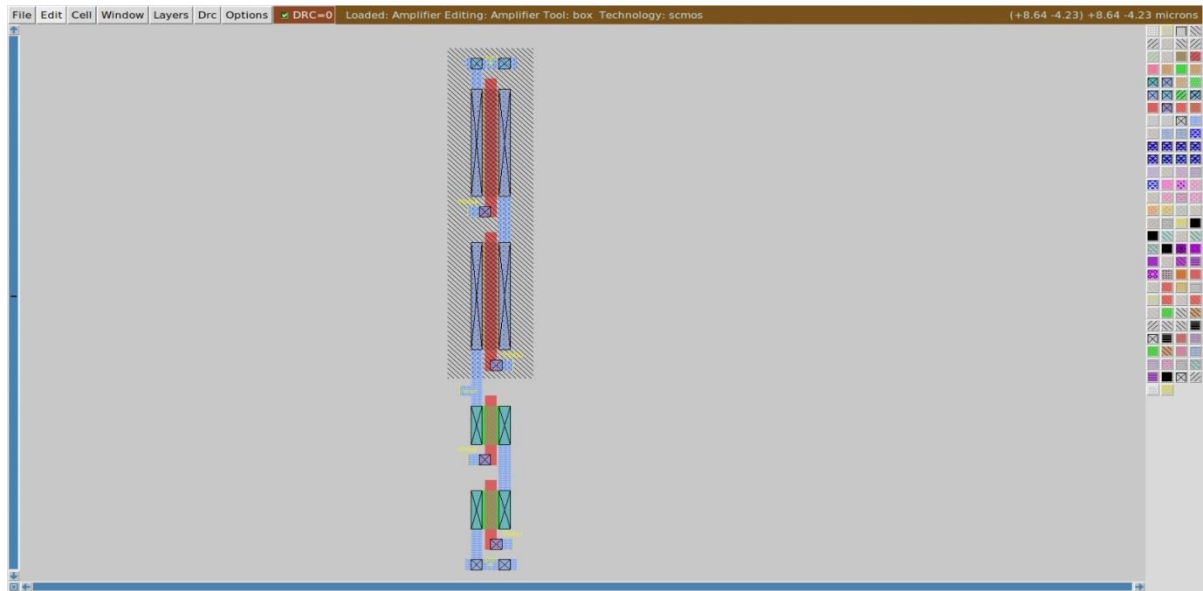

  
 
More zoomed images of cascode amplifier magic layout:



Current Mirror:

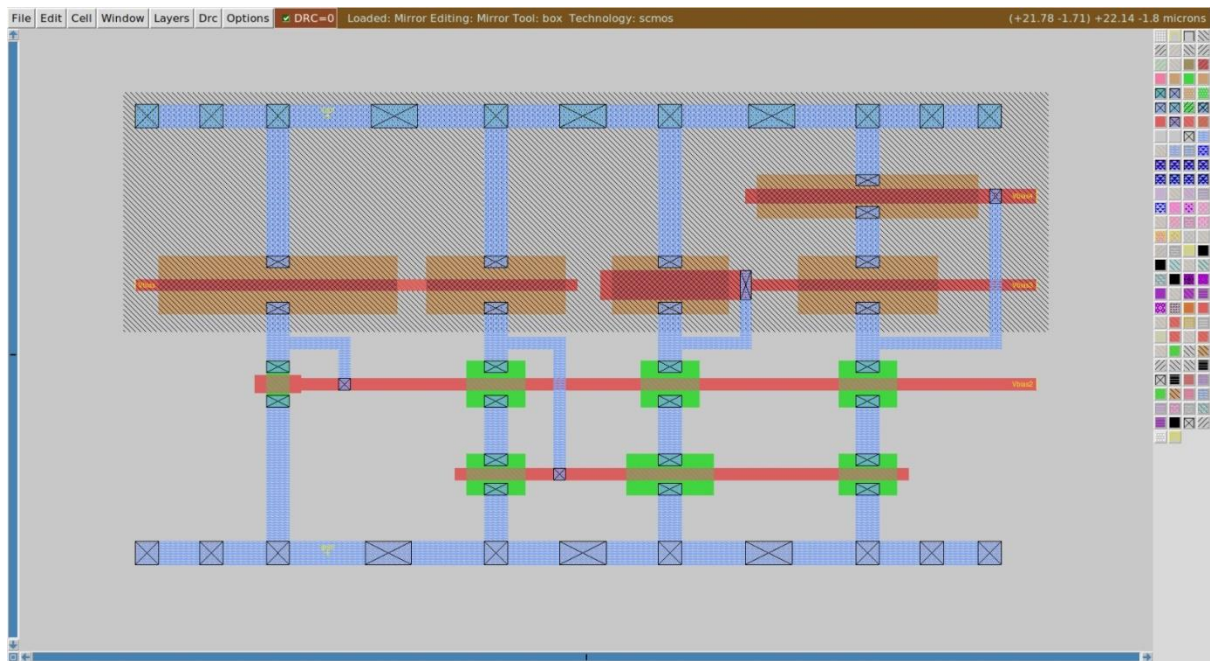

  Zoomed images of input and output terminals:



THANK YOU ☺